

# VLSI Design EE 523

## Spring 2026




**Shahid Masud**  
**Lecture 7**  
**LTSpice Examples**

# Topics for lecture 6

---

- MOS transistor theory and operation
- Mathematical Equations for:
  - Gate Capacitance, and charge stored
  - Velocity of electron forming current flow
  - W, L ratios in MOS
- Schokley model of MOSFET:
  - Equation for current  $I_{ds}$  in three regions of operation
- Quiz 1 today
- Readings: Chapter 2 of textbook

# MOS Transistor with Zero Bias Voltages

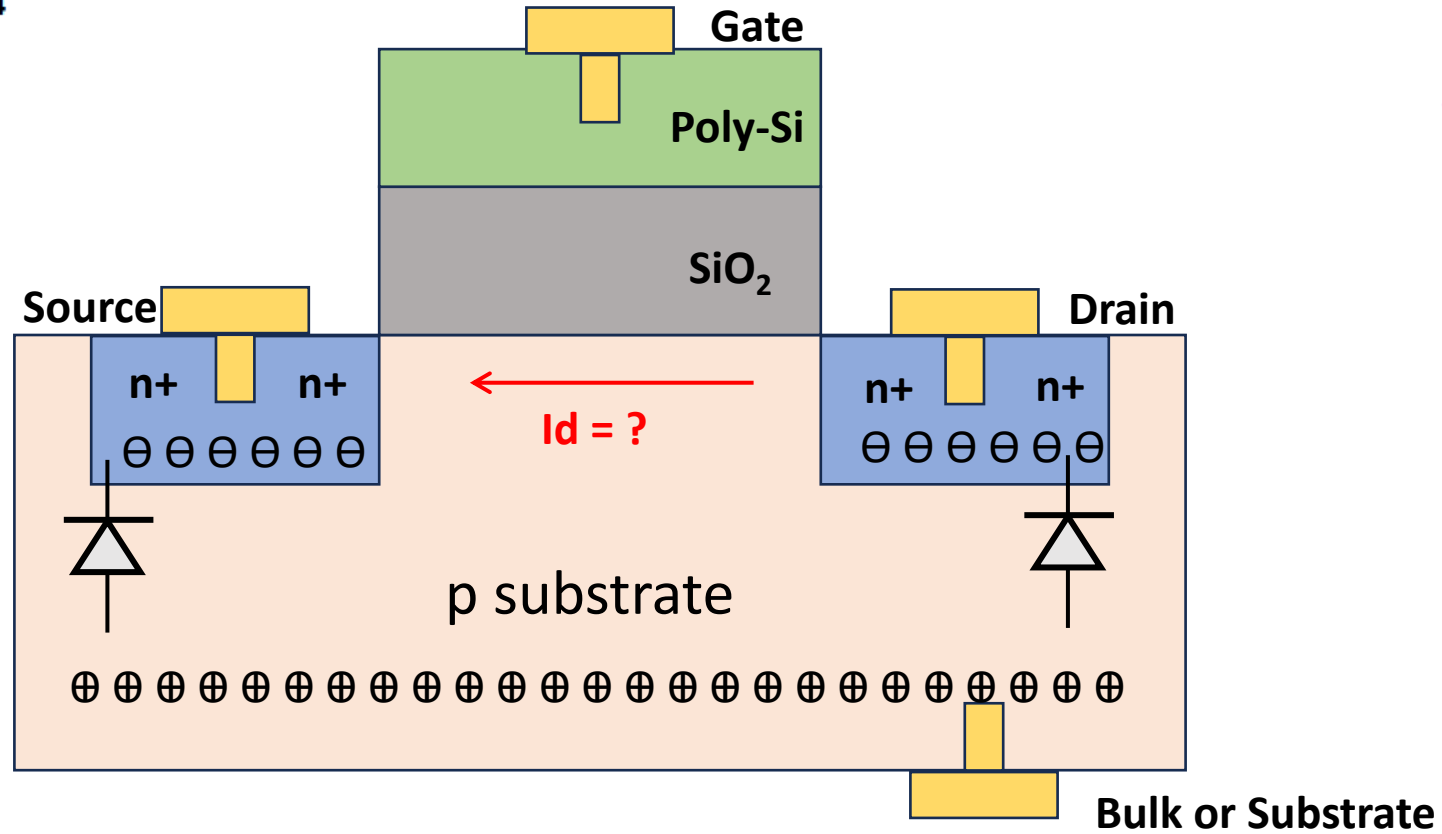  

# Shockley Model for CMOS Transistor


where

$$\beta = \mu C_{\text{ox}} \frac{W}{L}; V_{GT} = V_{gs} - V_t \quad (2.6)$$


EQ (2.10) summarizes the current in the three regions:

$$I_{ds} = \begin{cases} 0 & V_{gs} < V_t & \text{Cutoff} \\ \beta(V_{GT} - V_{ds}/2)V_{ds} & V_{ds} < V_{\text{dsat}} & \text{Linear} \\ \frac{\beta}{2}V_{GT}^2 & V_{ds} > V_{\text{dsat}} & \text{Saturation} \end{cases} \quad (2.10)$$

# CMOS Output Characteristics

 

(a)

 


(b)

**FIGURE 2.7** I-V characteristics of ideal  $4/2 \lambda$  (a) nMOS and (b) pMOS transistors

# Detailed Device Models

# Diode at a glance


## p-n junction diode

 

$$I_S \approx 10^{-15} \text{ A}$$

$$V_D \approx 0.7 \text{ V}$$


## Schottky diode

 

$$I_S \approx 10^{-7} \text{ A}$$

$$V_{SBD} \approx 0.3 \text{ V}$$

## Diode Forward Bias Characteristics

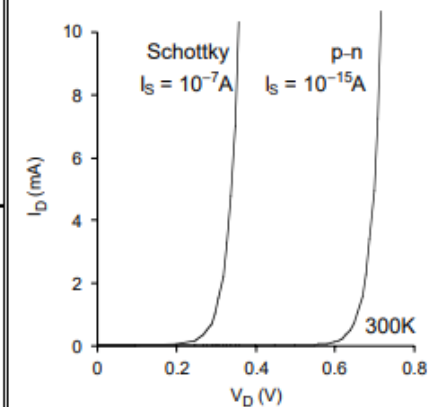

P-n junction diodes are rectifying and can be used as switches in logic gates. Schottky (metal-semiconductor) diodes are also rectifying but are faster switching due to the absence of minority carrier storage effects. Schottky diodes exhibit lower turn-on voltages than p-n junctions (~0.3V versus ~0.7V for silicon devices).


## Zero Bias Characteristics

$$V_{bi} = \frac{kT}{q} \ln \left( \frac{N_a N_d}{n_i^2} \right) \quad W = \sqrt{\frac{2 \epsilon_s V_{bi}}{q} \left( \frac{1}{N_a} + \frac{1}{N_d} \right)} \quad C_T = \frac{\epsilon_s A}{W} = A \sqrt{\frac{q \epsilon_s}{2 V_{bi}} \left( \frac{1}{N_a} + \frac{1}{N_d} \right)^{-1}}$$

## Forward Bias Characteristics

$$I = I_0 \left( e^{qV/kT} - 1 \right) \quad I_0 \approx \frac{qAD_n n_i^2}{N_a W_B} \text{ (short-base diode)}$$

## SPICE Model

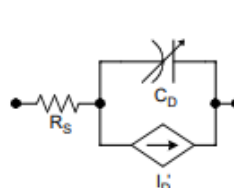

$$I'_D = I_S \left[ \exp \left( \frac{V'_D}{N V_T} \right) - 1 \right] \quad V_D = V'_D + I_D R_S$$


$$C_D = TT \frac{I_S}{N V_T} \exp \left( \frac{V'_D}{N V_T} \right) + \frac{CJO}{\left( 1 - \frac{V'_D}{VJ} \right)^M}$$

## Charge Control Model and Large Signal Switching Behavior


$$-i_n(0, t) = \frac{dQ_B}{dt} + \frac{Q_B}{\tau_F} - C_t \frac{dv}{dt} \quad t_s = \tau_F \left[ \left( 1 + \frac{I_F}{I_R} \right) - \left( 1 + \frac{\tau_R}{\tau_F} \right) \right]$$

$$f = 10^{-15} \quad p = 10^{-12} \quad n = 10^{-9} \quad \mu = 10^{-6} \quad m = 10^{-3} \quad k = 10^3 \quad M = 10^6 \quad G = 10^9$$

# NMOS Transistor W and L and Biasing

 


**FIGURE 7.1**  
Enhancement-type n-channel metal oxide–semiconductor field-effect transistor (MOSFET) and circuit symbol.

 


**FIGURE 7.7**  
N-channel enhancement-type MOSFET with bias.



# Characteristic curves of MOS

 


**FIGURE 7.7**  
N-channel enhancement-type MOSFET with bias.

 

**FIGURE 7.8**  
Characteristic curves for a MOSFET.

# Spice Model of MOS transistor

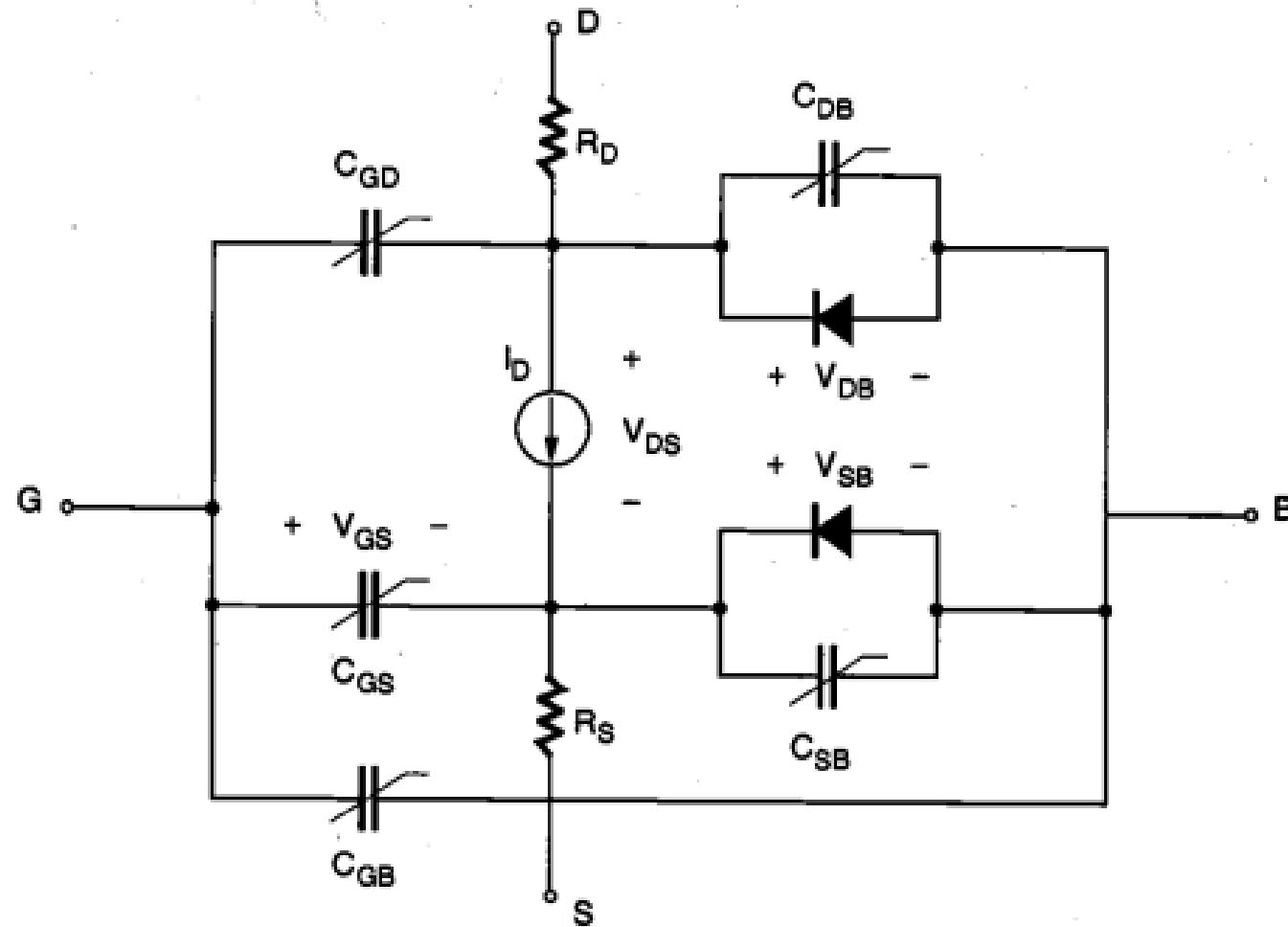

**Figure 4.1.** Equivalent circuit structure of the LEVEL 1 MOSFET model in SPICE.

## 4.2. The LEVEL 1 Model Equations

The LEVEL 1 model is the simplest current-voltage description of the MOSFET, which is basically the GCA-based quadratic model originally proposed by Shichman and Hodges. The equations used for the LEVEL 1 n-channel MOSFET model in SPICE are as follows.

### *Linear Region*

$$I_D = \frac{k'}{2} \cdot \frac{W}{L_{eff}} \cdot [2 \cdot (V_{GS} - V_T) V_{DS} - V_{DS}^2] \cdot (1 + \lambda V_{DS}) \quad \text{for } V_{GS} \geq V_T$$
$$\text{and } V_{DS} < V_{GS} - V_T \quad (4.1)$$

### *Saturation Region*

$$I_D = \frac{k'}{2} \cdot \frac{W}{L_{eff}} \cdot (V_{GS} - V_T)^2 \cdot (1 + \lambda \cdot V_{DS}) \quad \text{for } V_{GS} \geq V_T$$
$$\text{and } V_{DS} \geq V_{GS} - V_T \quad (4.2)$$

# Some parameters of NMOS Level 1 model

SPICE Level 1 Model Parameters for the MOSFET

Symbol	SPICE Name	Description	Units	Default	Typical
$K'$	KP	Process transconductance parameter	A/V <sup>2</sup>	1E-4	1E-4
$V_{TO}$	VTO	Threshold voltage with $V_{BS} = 0$	V	0	0.5
$\gamma$	GAMMA	Body effect coefficient	V <sup>1/2</sup>	0	1E-4
$2\phi_F$	PHI		V	1.0	1.0
$C_{GSO}$	CGSO	Gate-source capacitance per unit gate width	F/m	0	
$C_{GDO}$	CGDO	Gate-source capacitance per unit gate width	F/m	0	
$C_{GBO}$	CGBO	Gate-source capacitance per unit gate width	F/m	0	
$C_{BSO}$	CBSO	Gate-source capacitance per unit gate width	F/m	0	

# Some parameters of MOS Level 2 model

SPICE Level 2 model parameters for a typical 0.8  $\mu\text{m}$  CMOS process:


## .MODEL MODN NMOS LEVEL=2

```
+NLEV=0
+CGSO=0.350e-09    CGDO=0.350e-09    CGBO=0.150e-09
+CJ=0.300e-03      MJ=0.450e+00      CJSW=0.250e-09
+MJSW=0.330e+00    IS=0.000e+00      N=1.000e+00
+NDS=1.000e+12     VNDS=0.000e+00
+JS=0.010e-03      PB=0.850e+00      RSH=25.00e+00
+TOX=15.50e-09     XJ=0.080e-06
+VTO=0.850e+00     NFS=0.835e+12     NSUB=64.00e+15
+NEFF=10.00e+00    UTRA=0.000e+00
+UO=460.0e+00      UCRIT=38.00e+04    UEXP=0.325e+00
+VMAX=62.00e+03    DELTA=0.250e+00    KF=0.275e-25
+LD=0.000e-06      WD=0.600e-06      AF=1.500e+00
+BEX=-1.80e+00     TLEV=1.000e+00     TCV=1.400e-03
```

## .MODEL MODP PMOS LEVEL=2

```
+NLEV=0
+CGSO=0.350e-09    CGDO=0.350e-09    CGBO=0.150e-09
+CJ=0.500e-03      MJ=0.470e+00      CJSW=0.210e-09
+MJSW=0.290e+00    IS=0.000e+00      N=1.000e+00
+NDS=1.000e+12     VNDS=0.000e+00
+JS=0.040e-03      PB=0.800e+00      RSH=47.00e+00
+TOX=15.00e-09     XJ=0.090e-06
+VTO=-.725e+00     NFS=0.500e+12     NSUB=32.80e+15
+NEFF=2.600e+00    UTRA=0.000e+00
+UO=160.0e+00      UCRIT=30.80e+04    UEXP=0.350e+00
+VMAX=61.00e+03    DELTA=0.950e+00    KF=0.470e-26
+LD=-.075e-06      WD=0.350e-06      AF=1.600e+00
+BEX=-1.50e+00     TLEV=1.000e+00     TCV=-1.80e-03
```
 
## FIELD-EFFECT TRANSISTORS QUICK REFERENCE



The figure shows three schematic symbols for MOSFETs. The first is a Depletion n-MOSFET, represented by a vertical line with an arrow pointing out from the gate. The second is an Enhancement n-MOSFET, represented by a vertical line with an arrow pointing in to the gate. The third is an Enhancement p-MOSFET, represented by a vertical line with an arrow pointing out from the gate, similar to the depletion mode but with a different internal structure indicated by the gate symbol.

## n-MOSFET Modes of Operation

cutoff	$V_{GS} < V_T$	$I_D = 0$
linear	$V_{GS} > V_T$ $V_{GS} - V_T > V_{DS}$	$I_D = K \left[ (V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2} \right]$ $V_{DS} = (V_{GS} - V_T) - \sqrt{(V_{GS} - V_T)^2 - \frac{2I_D}{K}}$
saturation	$V_{GS} > V_T$ $V_{GS} - V_T < V_{DS}$	$I_D = \frac{K}{2} (V_{GS} - V_T)^2$

$$K_N = \frac{W_N}{L_N} k'_N \quad k'_N = \frac{\mu_n \epsilon_{ox}}{t_{ox}} \quad K_P = \frac{W_P}{L_P} k'_P \quad k'_P = \frac{\mu_p \epsilon_{ox}}{t_{ox}}$$

$$V_T = V_{TO} + GAMMA \left( \sqrt{PHI + V_{SB}} - \sqrt{PHI} \right)$$

$$I_D = \frac{KP}{2} \frac{\text{width}}{\text{length}} (V_{GS} - V_T)^2 (1 + V_{DS} \text{LAMBDA})$$

$$I_D = \frac{KP}{2} \frac{\text{width}}{\text{length}} \left[ (V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2} \right] (1 + V_{DS} \text{LAMBDA})$$


$$C_{GS} = width \times CGSO \quad C_{GD} = width \times CGDO \quad C_{GB} = width \times CGBO$$

$$C_{BD} = width \times CBDO \quad C_{BS} = width \times CBSO$$

$$\mu_n = 580 \text{ cm}^2 \text{ V}^{-1} \text{ s}^{-1} \quad \mu_p = 230 \text{ cm}^2 \text{ V}^{-1} \text{ s}^{-1} \quad \epsilon_{OX} = 3.9 \epsilon_0 \quad \lambda = 10^{-8} \text{ cm}$$


$$f = 10^{-15} \quad p = 10^{-12} \quad n = 10^{-9} \quad \mu = 10^{-6} \quad m = 10^{-3} \quad k = 10^3 \quad M = 10^6 \quad G = 10^9$$

# CMOS Inverter characteristics

 


**FIGURE 1.12**  
Voltage transfer characteristic for an inverter.

# OR gate using transmission gate logic

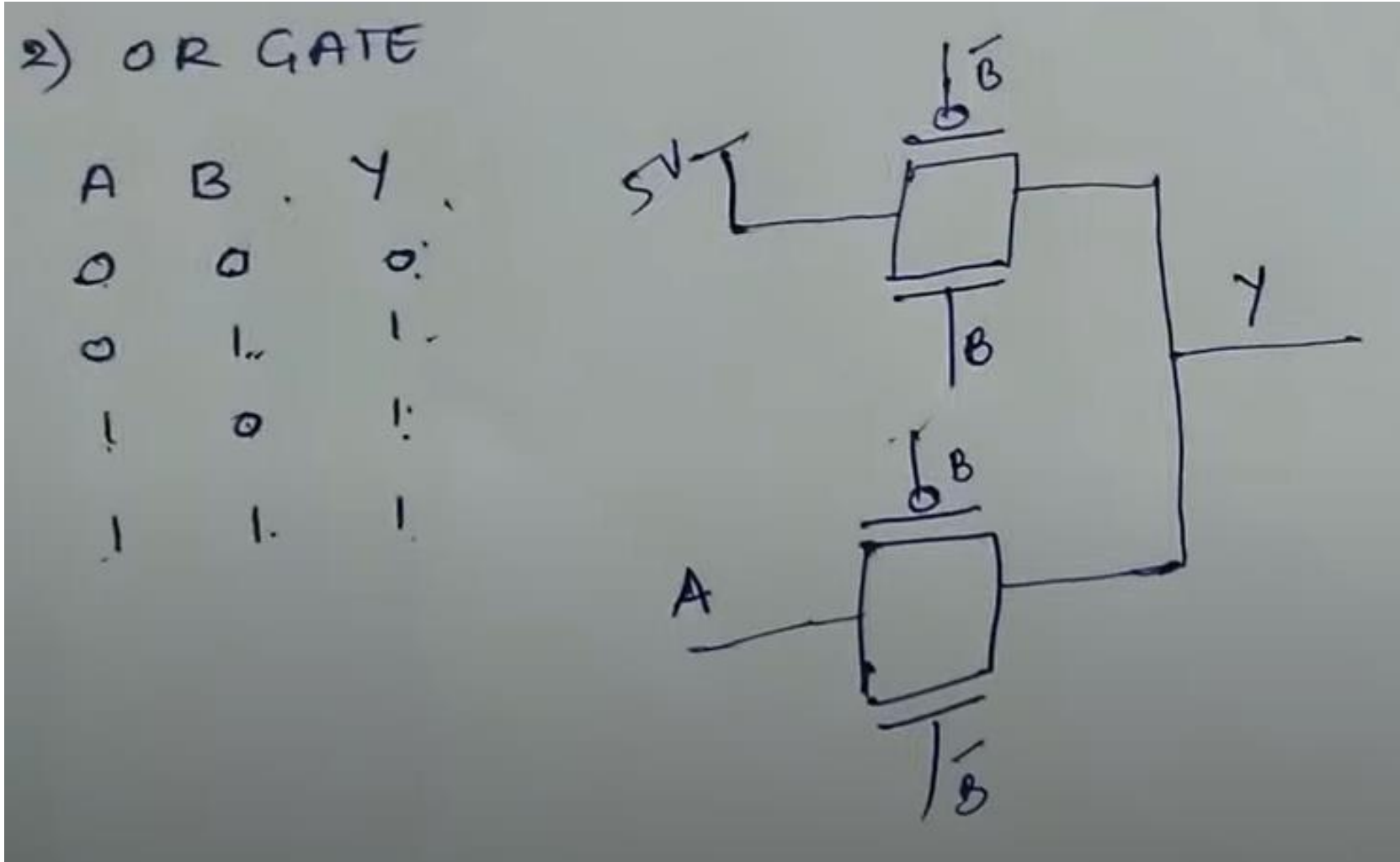



# Make a CMOS Inv based Oscillator

 

**FIGURE 1.16**

Seven-stage ring oscillator with a buffered output.

# Important Parameters 0.18u

## 4.10 Summary

Useful technology parameters for 0.18  $\mu\text{m}$  CMOS:


$$\begin{aligned}\mu_n &= 270 \text{ cm}^2/\text{V-s}, \quad \mu_p = 70 \text{ cm}^2/\text{V-s}, \quad t_{ox} = 35 \text{ \AA}, \\ C_{ox} &= 1.0 \text{ \mu F/cm}^2, \quad V_{TN} = 0.5 \text{ V}, \quad V_{TP} = -0.5 \text{ V} \\ E_{CN}L &= 1.2 \text{ V}, \quad E_{CP}L = 4.8 \text{ V}, \quad v_{sat} = 8 \times 10^6 \text{ cm/s}, \\ V_{DD} &= 1.8 \text{ V}, \quad 2|\phi_F| = 0.85 \text{ V}, \quad \gamma = 0.3 \text{ V}^{1/2}, L = 2\lambda = 200 \text{ nm}\end{aligned}$$

Useful technology parameters for 0.13  $\mu\text{m}$  CMOS:



$$\begin{aligned}\mu_n &= 270 \text{ cm}^2/\text{V-s}, \quad \mu_p = 70 \text{ cm}^2/\text{V-s}, \quad t_{ox} = 22 \text{ \AA}, \\ C_{ox} &= 1.6 \text{ \mu F/cm}^2, \quad V_{TN} = 0.4 \text{ V}, \quad V_{TP} = -0.4 \text{ V} \\ E_{CN}L &= 0.6 \text{ V}, \quad E_{CP}L = 2.4 \text{ V}, \quad v_{sat} = 8 \times 10^6 \text{ cm/s}, \\ V_{DD} &= 1.2 \text{ V}, \quad 2|\phi_F| = 0.88 \text{ V}, \quad \gamma = 0.2 \text{ V}^{1/2}, L = 2\lambda = 100 \text{ nm}\end{aligned}$$

# Getting Started with LTSpice

# LTSpice Interface Startup Screen

 

# Make NMOS Circuit

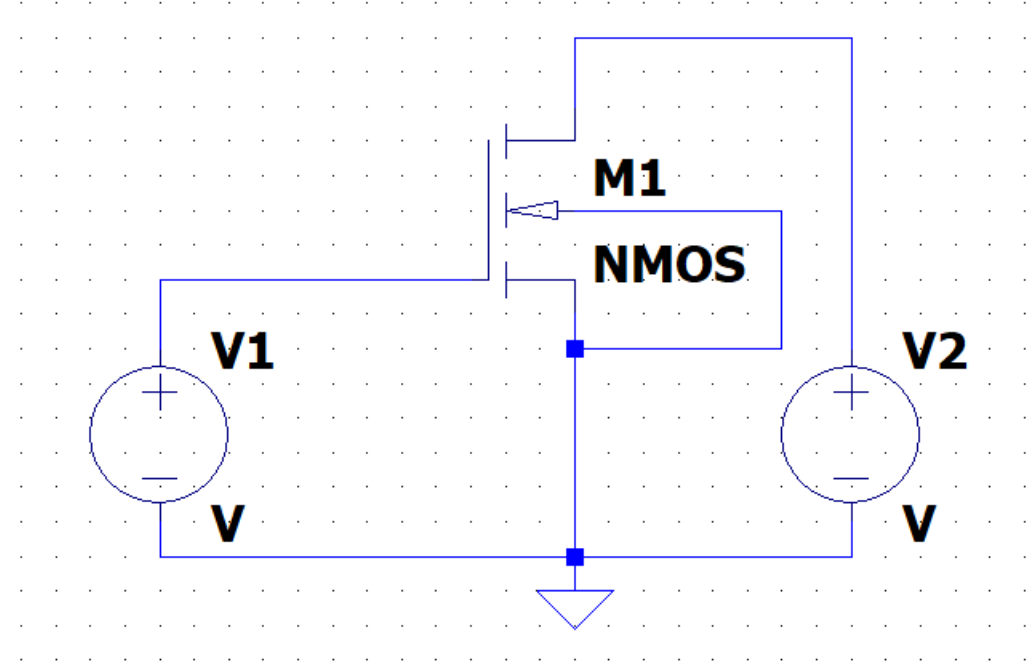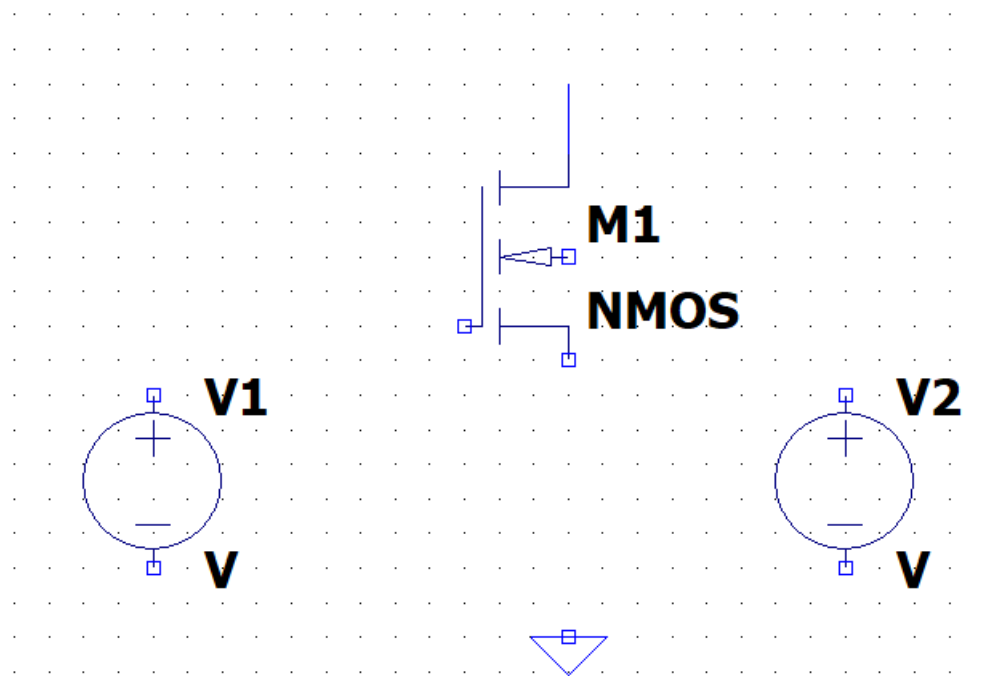

We can find NMOS (3 Terminal) and NMOS4 (4 Terminal) in the Default Component Library

## **Case 1: Default Component Library**

**Configure all voltage sources**

**Configure all devices e.g. transistors**

# Right Click on Voltage Source → Advanced

### Voltage Source - V1

DC value[V]:

Series Resistance[Ω]:

OK

Cancel

Advanced

### Independent Voltage Source - V1

Functions

- ☒ (none)
- ☐ PULSE(V1 V2 Tdelay Trise Tfall Ton Period Ncycles)
- ☐ SINE(Voffset Vamp Freq Td Theta Phi Ncycles)
- ☐ EXP(V1 V2 Td1 Tau1 Td2 Tau2)
- ☐ SFFM(Voff Vamp Fcar MDI Fsig)
- ☐ PWL(t1 v1 t2 v2...)
- ☐ PWL FILE:  Browse

Additional PWL Points

Make this information visible on schematic: ☒

DC Value

DC value:

Make this information visible on schematic: ☒

Small signal AC analysis(.AC)

AC Amplitude:

AC Phase:

Make this information visible on schematic: ☒

Parasitic Properties

Series Resistance[Ω]:

Parallel Capacitance[F]:

Make this information visible on schematic: ☒

Cancel

OK

# Right Click on NMOS Transistor to Configure

**Monolithic MOSFET - M1**

Model Name:

Length(L):

Width(W):

Drain Area(AD):


Source Area(AS):

Drain Perimeter(PD):

Source Perimeter(PS):

No. Parallel Devices(M):

NMOS

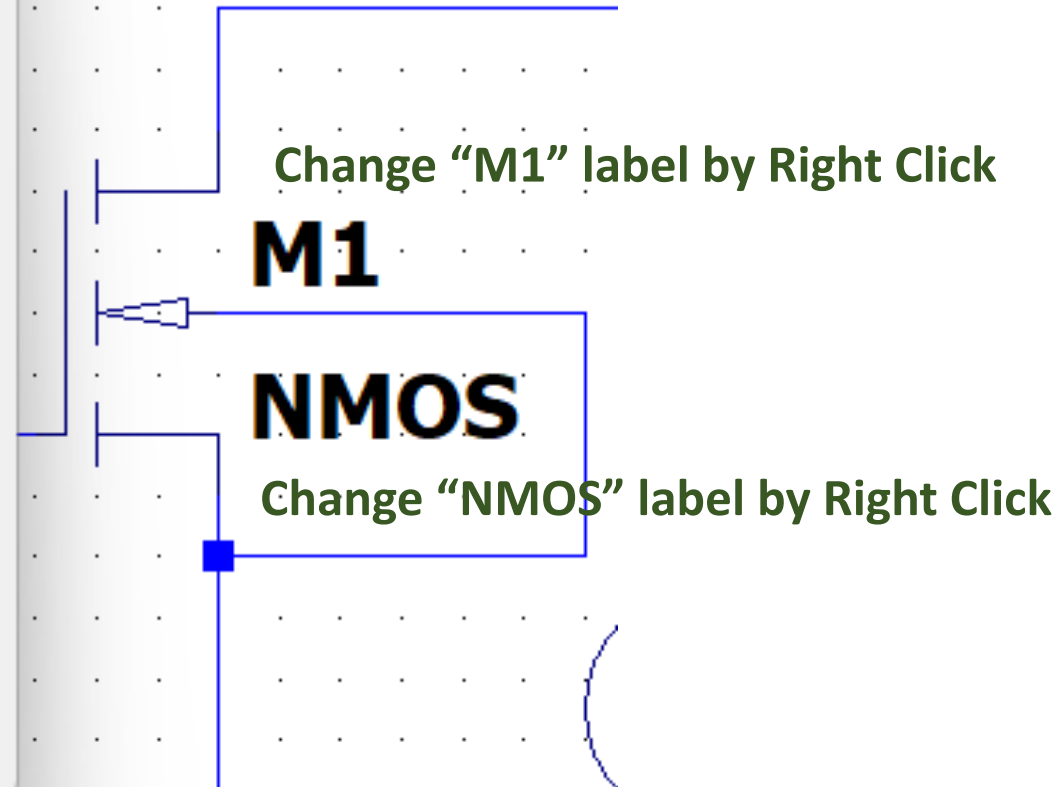


















# Adding Device Models for VLSI

- Make a working folder on Desktop
- Put model files in this folder
- You can configure paths and colours in Tools → Settings
- Some model file needs to be included In the Spice Deck

Model files Highlighted text files in folder

 tsmc180nmos	05-Feb-2024 10:13 pm	Static Library	6 KB
 65nm_bulk	09-Feb-2025 12:33 pm	Text Document	10 KB
 130nm_bulk	09-Feb-2025 12:33 pm	Text Document	10 KB
 CMOS_Inv_PropDelay1	10-Feb-2025 5:00 pm	Text Document	2 KB
 CMOS_Inv1	10-Feb-2026 6:46 pm	Text Document	1 KB
 CMOS_Inv2	10-Feb-2025 11:55 am	Text Document	1 KB
 CMOS_Nand1	10-Feb-2025 11:59 am	Text Document	2 KB
 cmosedu_models	03-Feb-2024 7:44 pm	Text Document	12 KB
 NMOS_Char1	10-Feb-2026 7:00 pm	Text Document	1 KB
 NMOS_Char2	10-Feb-2026 10:24 pm	Text Document	1 KB
 nmos_outputch1	09-Feb-2025 11:24 am	Text Document	1 KB
 OR_PassTrans1	10-Feb-2025 12:03 pm	Text Document	1 KB
 PMOS_Char1	10-Feb-2025 11:39 am	Text Document	2 KB
 pmos_outputch1	10-Feb-2025 11:40 am	Text Document	1 KB
 tsmc180	10-Feb-2026 10:05 pm	Text Document	6 KB

# How do Device Model files look like

---

## Examine cmosedu\_models.txt file

We find following models:

.MODEL N\_1u NMOS LEVEL = 3

.MODEL P\_1u PMOS LEVEL = 3

.model N\_50n nmos level = 54

.model P\_50n pmos level = 54

## Examine tsmc180.txt file

We find following models:

.MODEL NMOS NMOS (LEVEL = 49

.MODEL PMOS PMOS (LEVEL = 49

.model N\_50n nmos level = 54

.model P\_50n pmos level = 54

Examine other model files:

tsmcnmcmos.lib

130nm\_bulk.txt

.....

So on

# How to add in LTSpice and Do Basic Simulations

---

- Use Spice Directive

**.inc cmosedu\_models.txt**

- FOR Transistor Characteristics
- We need to SWEEP VDS and VGS and get NMOS operating curves
- Use either these Spice Directives:
  - **Approach 1:** Give DC Sweep to both voltages

**.dc VDS 0 2.5 0.1 VGS 0 2.5 0.25**

- **Approach 2:** Give a variable name {VGIN} to VGS, use .STEP and .dc

**.dc VDS 0 1.8 0.1**


**.STEP PARAM VGIN 0.0 1.8 0.2**

# Examples of Sweeping Voltages

Blue text is 'Comment'


`.inc cmosedu_models.txt`

`.dc VDS 0 2.5 0.1 VGS 0 2.5 0.25`

 

Use `.STEP Param {voltage name}` to vary both VGS and VDS  
models in `cmosedu_models.txt` are N\_1u N\_50n P\_1u P\_50n

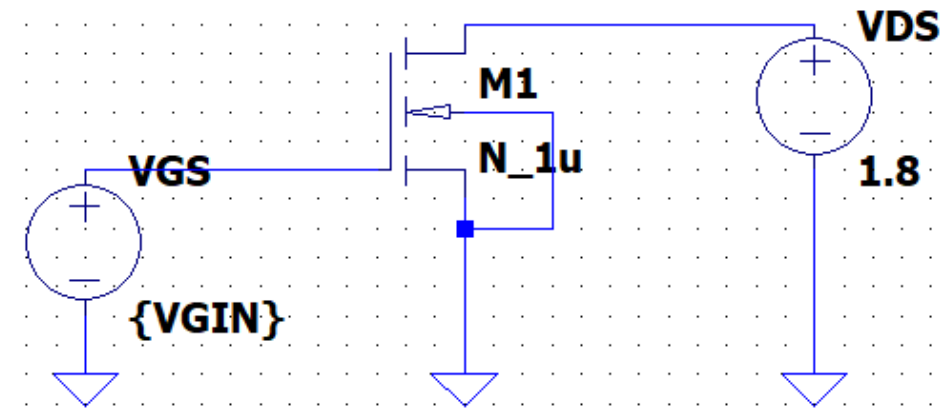NMOS Characterization with different model files



`.inc cmosedu_models.txt`

`.dc VDS 0 1.8 0.1`





`.STEP PARAM VGIN 0.0 1.8 0.2`

`tsmc180nmos.lib` contains `.MODEL TSMC180nmN NMOS`

`.inc tsmc180nmos.lib`
 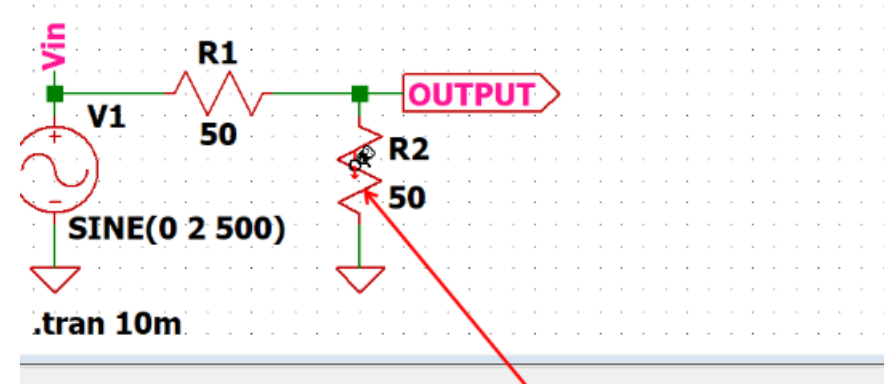  
# How to Simulate and View Waveforms



- Press Green Triangle to 'RUN' simulation
- A blank window will appear over the circuit
- Bring cursor over a wire or a source
- Either voltage probe or current probe will show
- Pressing mouse will select that value for display



**Move the cursor to R2 to change to a current probe**

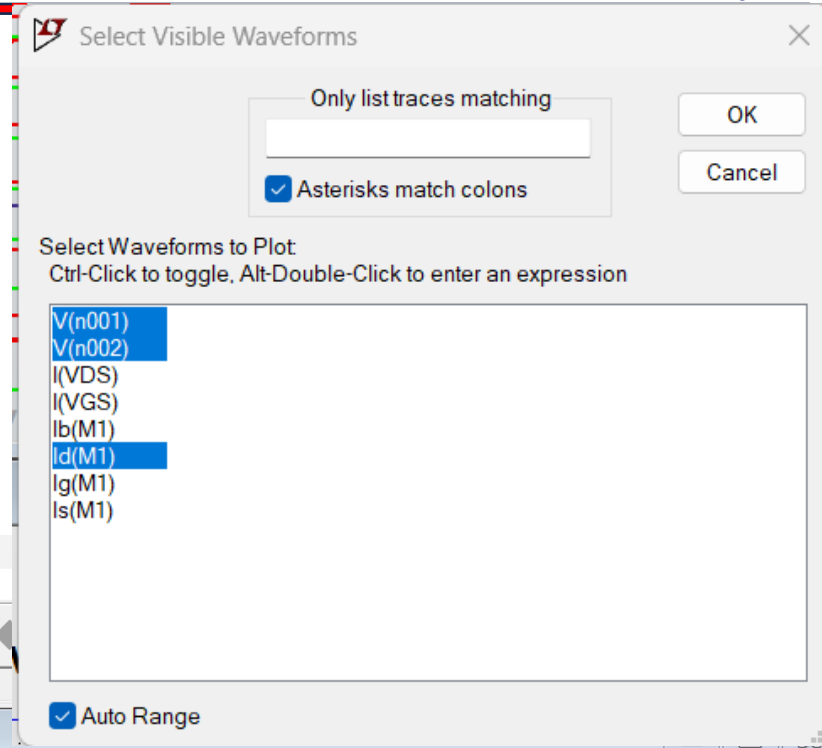 
# Waveform Display – As selected by Probes

**Use View → Visible Traces**  
**Select the Waveforms that you want to Display**



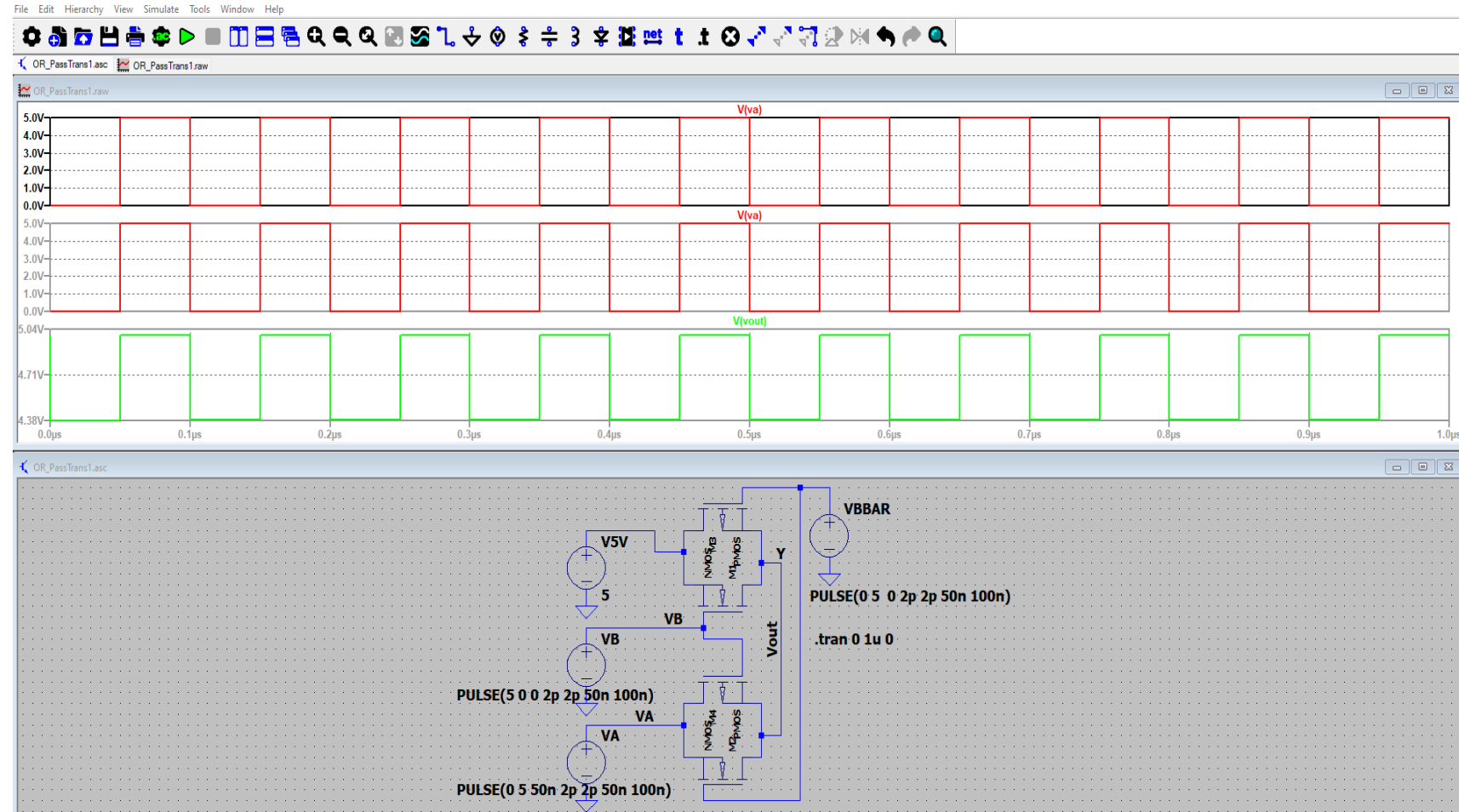
# View Plots in Separate Window Panes

After Running Simulation:  
Right Click on Waveform Window  
There is option to Add new pane  
First click on new pane and then  
Add wave through probe on circuit



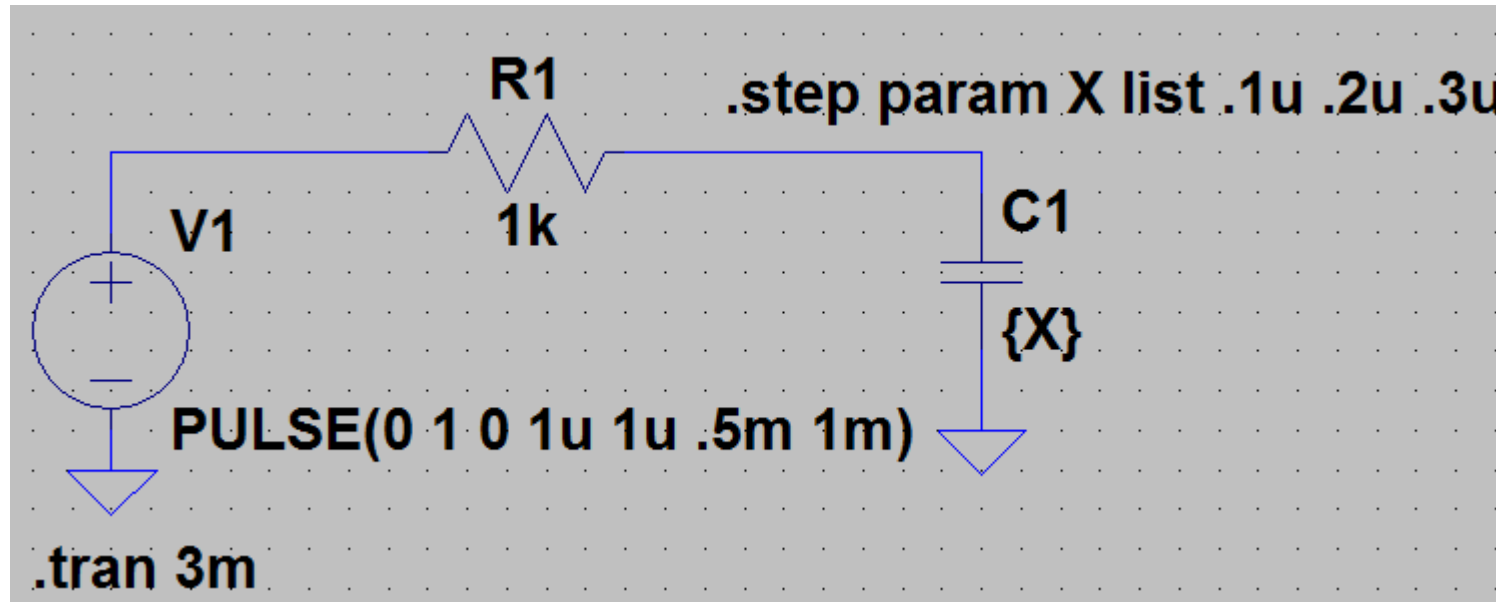
# Different Values can be Stepped using .STEP





# Different types of Circuit Analysis

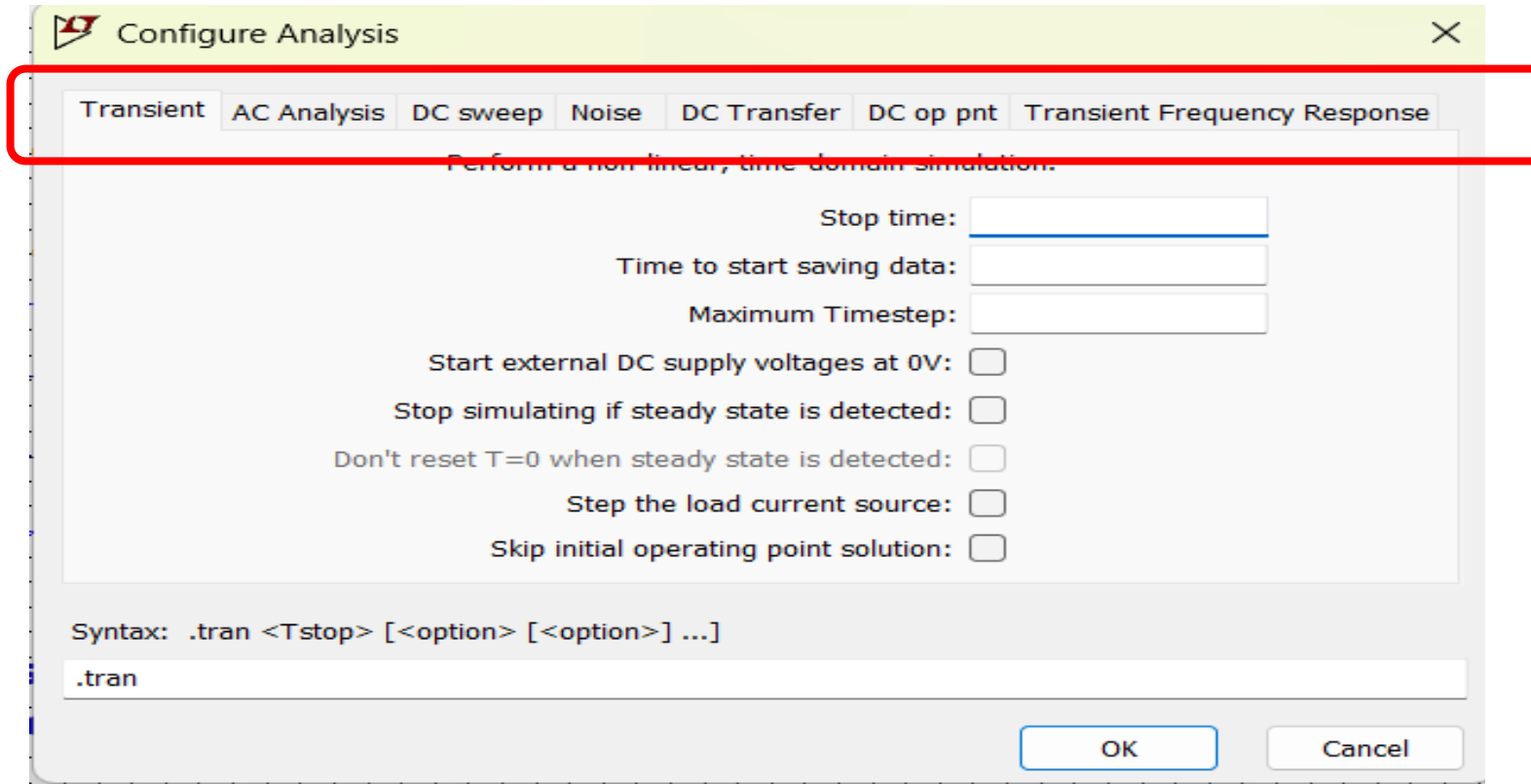

<https://www.allaboutcircuits.com/technical-articles/how-to-perform-transient-analysis-noise-simulation-LTspice/>

<https://www.cxi1.co.uk/ltspice/transient.htm>

<https://www.allaboutcircuits.com/technical-articles/intermediate-ltspice-tutorial/>

<https://www.allaboutcircuits.com/technical-articles/basic-circuit-simulation-with-ltspice/>

[LTspice XVII Tutorial | Spiceman](#)

# .meas statement for waveforms

[.measure/.meas : LTspice -- Evaluate User-Defined Electrical Quantities | Spiceman](#)

## .meas Command in LTSpice 1

The `.meas` command in LTSpice is used to measure specific parameters or values during a simulation, such as voltages, currents, or time intervals. It allows you to extract and analyze results programmatically.

### Example: Measuring Rise Time

To measure the rise time of a signal `V(out)` when it crosses 0.5V:

```
meas trise when v(out)=0.5 rise=1
```

This command calculates the time at which `V(out)` first rises to 0.5V.

### Example: Measuring Time Period

To measure the time period of a clock signal:

```
meas trise1 when v(clk)=0.5 rise=1
meas trise2 when v(clk)=0.5 rise=2
meas T param trise2 - trise1
```

Here, `T` represents the time period of the clock signal by subtracting the first rise time from the second.

### Example: Finding Voltage at Specific Time

To find the voltage at a specific point in time (e.g., at `tfall`):

```
meas tfall when v(out)=0.5 fall=1
meas Vout find v(out) at tfall
```

This measures the voltage `V(out)` at the falling edge of the signal.

### Key Considerations:

- **Syntax:** `.meas <name> <operation> <signal> [conditions]`
- **Operations:** `find`, `param`, etc.
- **Conditions:** Use `when`, `rise=n`, or `fall=n` to specify criteria.
- Ensure proper signal naming and conditions for accurate measurements.
- Use `.step` with `.meas` for parameter sweeps across multiple simulations.

The `.meas` command is versatile and essential for automating measurements in LTSpice simulations.

- Textbook Chapter